

CSE/EE – 7387
DIGITAL SYSTEMS DESIGN
FINAL PROJECT REPORT
ON
MATRIX MULTIPLICATION

Done by,
Arjun Ajit Warty
STUDENT # 47319796
Department of Electrical Engineering
Southern Methodist University

ASSIGNMENT DATE: DEC 07, 2017
DUE ON: DEC 07, 2017
SUBMISSION DATE: DEC 07, 2017

Table of Contents

OBJECTIVE:	3
CONCEPT FOR DESIGN	3
Matrix Multiplication Concept:	3
THE DESIGN	4
SCHEDULING TABLE	4
DATA PATH	5
DESIGN OF MAC AND MAC CONTROLLER	5
MAC SHEMATIC FOR MATRIX MULTIPLICATION	5
MAC CONTROLLER VERILOG	6
DESIGN OF INPUT REGISTERS AND INPUT CONTROLLER	6
INPUT REGISTER SCHEMATIC	6
INPUT CONTROLLER VERILOG	7
DESIGN OF OUTPUT CONTROLLER AND OUTPUT REGISTER	7
OUTPUT REGISTER SCHEMATIC	7
OUTPUT CONTROLLER VERILOG	8
MATRIX MULTIPLIER DESIGN	8
Functionality Claims	9
For Altera Cyclone EP1C3T100A8	9
SIMULATION REPORT	9
REGISTER TO REGISTER DELAY REPORT	9
For Altera MAXII EPM1270F256A5	10
SIMULATION REPORT	10
REGISTER TO REGISTER DELAY REPORT	10
ASM CHART	10
INPUT CONTROLLER	10
MAC CONTROLLER	11
OUTPUT CONTROLLER	11
PROBLEMS FACED	12
CONCLUSION	12

OBJECTIVE:

The objective of this project is to implement a circuit that will multiply a 3x4 matrix with its transpose. That is, the circuit will compute B where $B = A^T \cdot A$. Each matrix element, a_{ij} is in 8-bit, 2's complement form.

CONCEPT FOR DESIGN

Mathematically the function of this circuit is shown in the image below with its equation.

Equation: $B = A^T \cdot A$

A^T				A					B			
a_{11}	a_{21}	a_{31}		a_{11}	a_{12}	a_{13}	a_{14}	=	b_{11}	b_{12}	b_{13}	b_{14}
a_{12}	a_{22}	a_{32}	X	a_{21}	a_{22}	a_{23}	a_{24}		b_{21}	b_{22}	b_{23}	b_{24}
a_{13}	a_{23}	a_{33}		a_{31}	a_{32}	a_{33}	a_{34}		b_{31}	b_{32}	b_{33}	b_{34}
a_{14}	a_{24}	a_{34}							b_{41}	b_{42}	b_{43}	b_{44}

Matrix Multiplication Concept:

Equation for Matrix Multiplication is a very simple equation but yet it one of the hardest to implement in a circuit with restrictions. The Equation for Matrix Multiplication is given below

$$b_{11} = a_{11} * a_{11} + a_{21} * a_{21} + a_{31} * a_{31}$$

$$b_{12} = a_{11} * a_{12} + a_{21} * a_{22} + a_{31} * a_{32}$$

$$b_{13} = a_{11} * a_{13} + a_{21} * a_{23} + a_{31} * a_{33}$$

$$b_{14} = a_{11} * a_{14} + a_{21} * a_{24} + a_{31} * a_{34}$$

$$b_{22} = a_{12} * a_{12} + a_{22} * a_{22} + a_{32} * a_{32}$$

$$b_{23} = a_{12} * a_{13} + a_{22} * a_{23} + a_{32} * a_{33}$$

$$b_{24} = a_{12} * a_{14} + a_{22} * a_{24} + a_{32} * a_{34}$$

$$b_{33} = a_{13} * a_{13} + a_{23} * a_{23} + a_{33} * a_{33}$$

$$b_{34} = a_{13} * a_{14} + a_{23} * a_{24} + a_{33} * a_{34}$$

$$b_{44} = a_{14} * a_{14} + a_{24} * a_{24} + a_{34} * a_{34}$$

Thus, we have our 10 coefficients for the matrix B but the remaining six do not need to be calculated as they are equal to the other six coefficients namely, $b_{21} = b_{12}$, $b_{13} = b_{31}$, $b_{14} = b_{41}$, $b_{23} = b_{32}$, $b_{24} = b_{42}$, $b_{34} = b_{43}$.

THE DESIGN

We are able to implement the functionality of a Matrix Multiplier in Quartus II – Altera through many different techniques, but we always need to know the starting point of the project and that for me was the Scheduling Table.

SCHEDULING TABLE

My entire design is based on the table shown below. We only need to calculate 10 values, because not every of the 16 values are different. As the table shows, the initiation rate is 19 clock cycles and the latency is 28 cycles.

Clock Cycle	I/P	MAC	Output of MAC	Output
0	Initial State			
1	a11			
2	a21			
3	a31			
4	a12			
5	a22			
6	a32			
7	a13			
8	a23			
9	a33			
10	a14	$b_{11} = a_{11} * a_{11} + a_{21} * a_{21} + a_{31} * a_{31}$	b1	
11	a24	$b_{12} = a_{11} * a_{12} + a_{21} * a_{22} + a_{31} * a_{32}$	b2	
12	a34	$b_{13} = a_{11} * a_{13} + a_{21} * a_{23} + a_{31} * a_{33}$	b3	
13		$b_{14} = a_{11} * a_{14} + a_{21} * a_{24} + a_{31} * a_{34}$	b4	output_rdy=1
14		$b_{22} = a_{12} * a_{12} + a_{22} * a_{22} + a_{32} * a_{32}$	b5	b11
15		$b_{23} = a_{12} * a_{13} + a_{22} * a_{23} + a_{32} * a_{33}$	b6	b12
16		$b_{24} = a_{12} * a_{14} + a_{22} * a_{24} + a_{32} * a_{34}$	b7	b13
17		$b_{33} = a_{13} * a_{13} + a_{23} * a_{23} + a_{33} * a_{33}$	b8	b14
18		$b_{34} = a_{13} * a_{14} + a_{23} * a_{24} + a_{33} * a_{34}$	b9	b12
19	clear	$b_{44} = a_{14} * a_{14} + a_{24} * a_{24} + a_{34} * a_{34}$	b10	b22
20	a11			b23
21	a21			b24
22	a31			b13
23	a12			b23
24	a22			b33
25	a32			b34
26	a13			b14
27	a23			b24
28	a33			b34
29	a14			b44

DATA PATH

Once the Scheduling Table for the design was complete I had to start working on the designing a Data Path for my concept to work and shown below is the Data Path Diagram for the above concept.

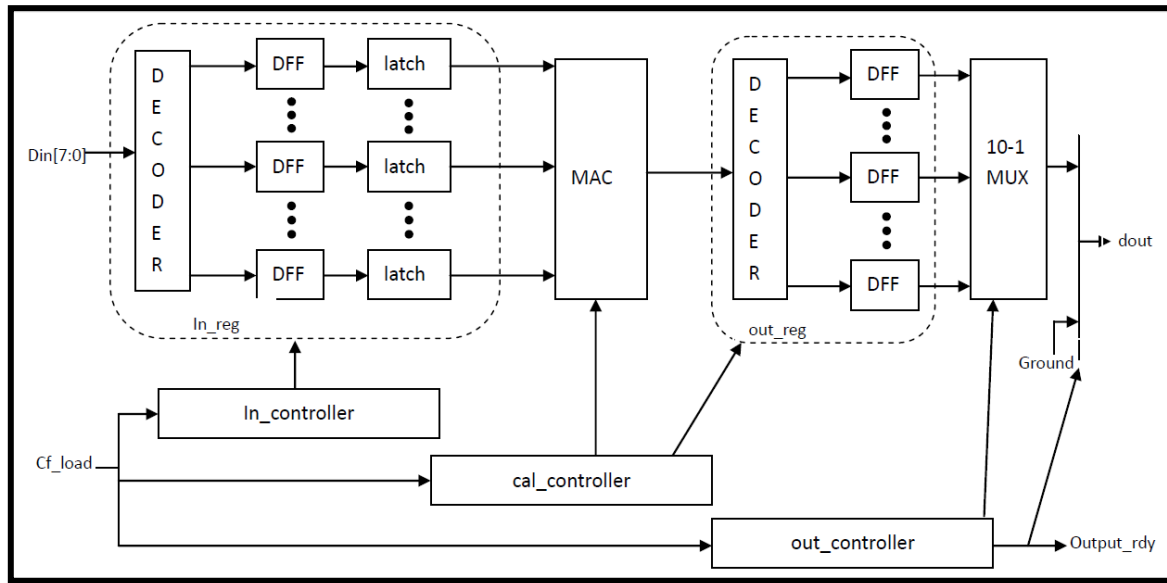


FIG. 1 : DATA PATH DIAGRAM

DESIGN OF MAC AND MAC CONTROLLER

MAC SCHEMATIC FOR MATRIX MULTIPLICATION

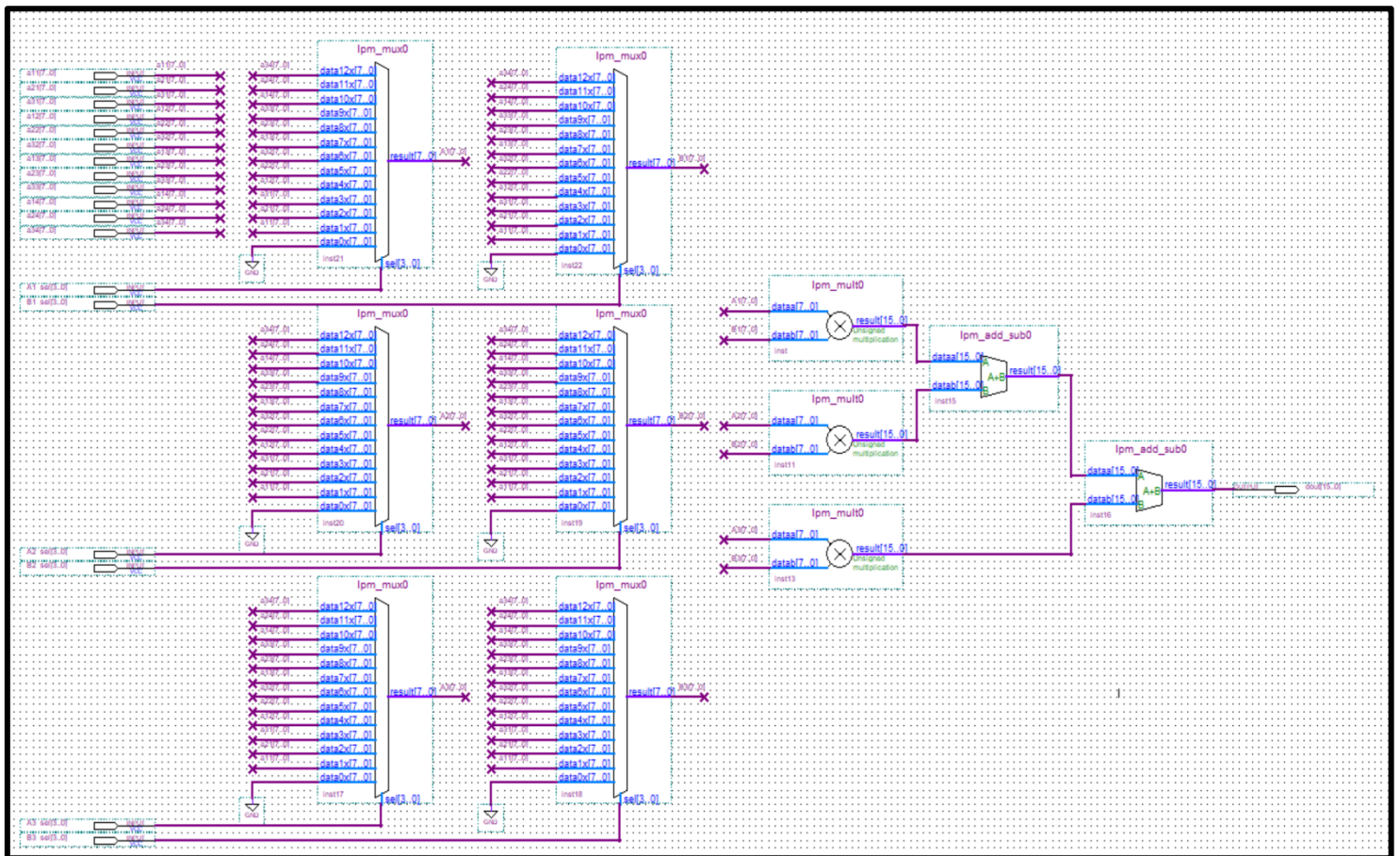


FIG. 2 : MAC UNIT SCHEMATIC

The MAC unit is designed to perform the arithmetic operations to the inputs provided by the input register and give the output to the output register.

MAC CONTROLLER VERILOG

The design for the MAC is stored in the MAC_CONTROLLER. V file in the folder along with its block diagram.

```

1 module MAC_CONTROLLER(reset, CLK, cf_load, a1, b1, a2, b2, a3, b3, sclr, output_select);
2 input cf_load, reset, CLK;
3 output reg [3:0] a1,b1;
4 output reg [3:0] a2,b2;
5 output reg [3:0] a3,b3;
6 output sclr;
7 output reg [3:0] output_select; //10 output value
8 reg [4:0] pstate;
9 reg [4:0] nstate;
10 parameter s0 = 5'b00000, s1 = 5'b00001, s2 = 5'b00010, s3 = 5'b00011,
11 s4 = 5'b00100, s5 = 5'b00101, s6 = 5'b00110, s7 = 5'b00111,
12 s8 = 5'b01000, s9 = 5'b01001, s10 = 5'b01010, s11 = 5'b01011,
13 s12 = 5'b01100, s13 = 5'b01101, s14 = 5'b01110, s15 = 5'b01111,
14 s16 = 5'b10000, s17 = 5'b10001, s18 = 5'b10010, s19 = 5'b10011,
15 s20 = 5'b10100, s21 = 5'b10101, s22 = 5'b10110;
16
17 always@(posedge CLK or posedge reset )
18 if (reset == 1'b1)
19 pstate <= s0;
20 else
21 pstate <= nstate;
22
23 always@(pstate or cf_load)
24 begin
25 a1 <= 4'b0;
26 a2 <= 4'b0;
27 a3 <= 4'b0;
28 b1 <= 4'b0;
29 b2 <= 4'b0;
30 b3 <= 4'b0;
31 output_select [3:0] <= 4'b0;

```

FIG. 3 : MAC CONTROLLER CODE

DESIGN OF INPUT REGISTERS AND INPUT CONTROLLER

INPUT REGISTER SCHEMATIC

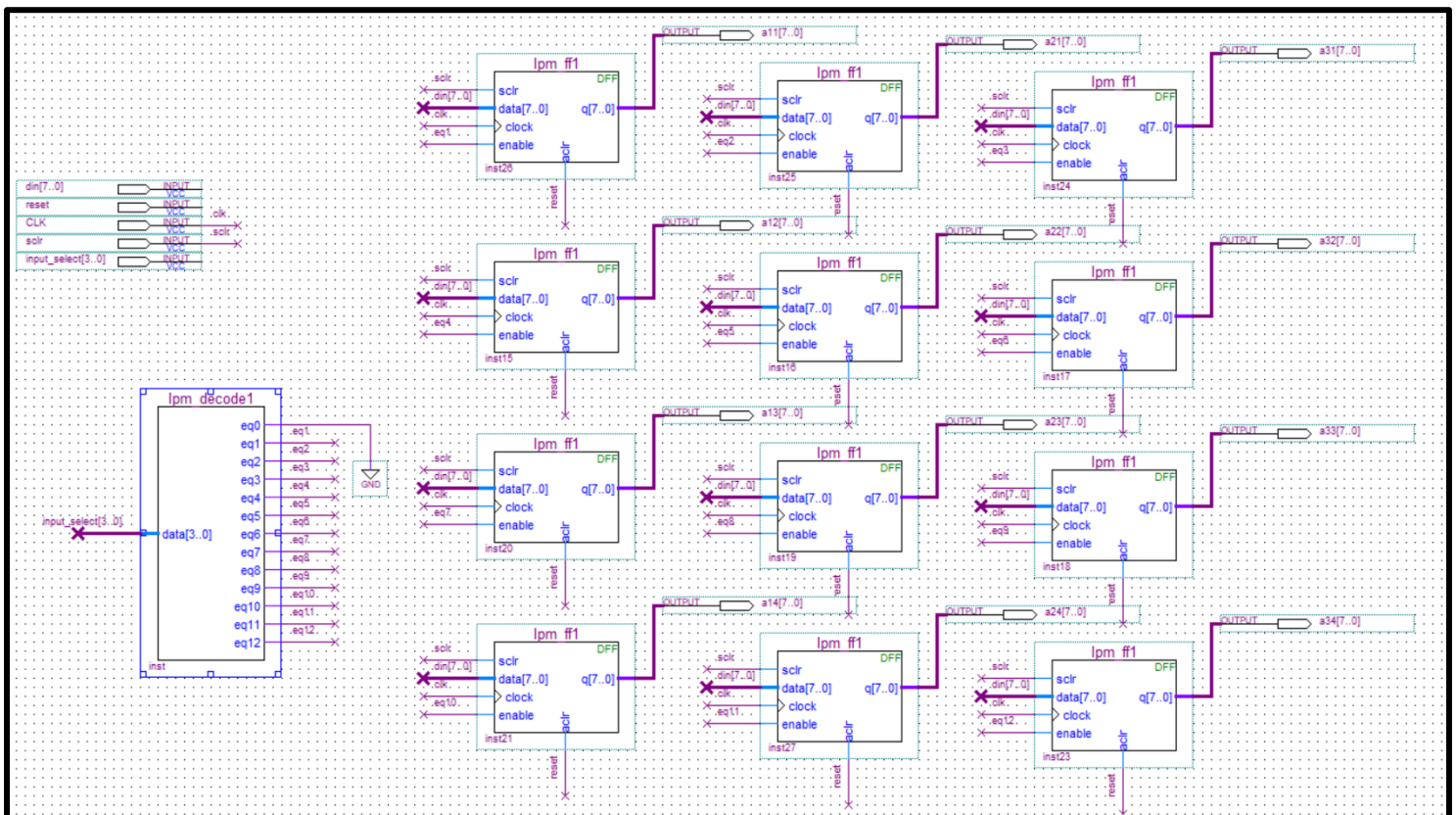


FIG. 4 : INPUT REGISTER SCHEMATIC

All the data coming from the source goes into goes to the Input Registers which are made up of twelve 8-bit D-FF. The decoder is used to select the D-FF in which we store coefficient of the input matrix.

INPUT CONTROLLER VERILOG

```

1 module INPUT_CONTROLLER(reset, clk, cf_load, clr, gate, input_sel);
2   input  cf_load, reset, clk;           //input
3   output clr;
4   output reg [3:0] gate;               //12 input reg
5   output reg input_sel;
6   reg [4:0] pstate, nstate;
7
8   parameter s0 = 5'b00000, s1 = 5'b00001, s2 = 5'b00010, s3 = 5'b00011,
9             s4 = 5'b00100, s5 = 5'b00101, s6 = 5'b00110, s7 = 5'b00111,
10            s8 = 5'b01000, s9 = 5'b01001, s10 = 5'b01010, s11 = 5'b01011,
11            s12 = 5'b01100, s13 = 5'b01101, s14 = 5'b01110, s15 = 5'b01111,
12            s16 = 5'b10000, s17 = 5'b10001, s18 = 5'b10010, s19 = 5'b10011;
13                                     //20 state, including 1 initiation state
14
15   always@(posedge clk or posedge reset)
16   begin
17     if (reset == 1'b1)
18       pstate <= s0;
19     else
20       pstate <= nstate;
21   end
22
23   always@(pstate or cf_load)         //state transform
24   begin
25     gate [3:0] <= 4'b0;
26     input_sel <= 0;
27   end
28
29   case(pstate)
30     s0: begin
31       if (cf_load == 1'b1)

```

FIG. 5 : INPUT CONTROLLER CODE

DESIGN OF OUTPUT CONTROLLER AND OUTPUT REGISTER

OUTPUT REGISTER SCHEMATIC

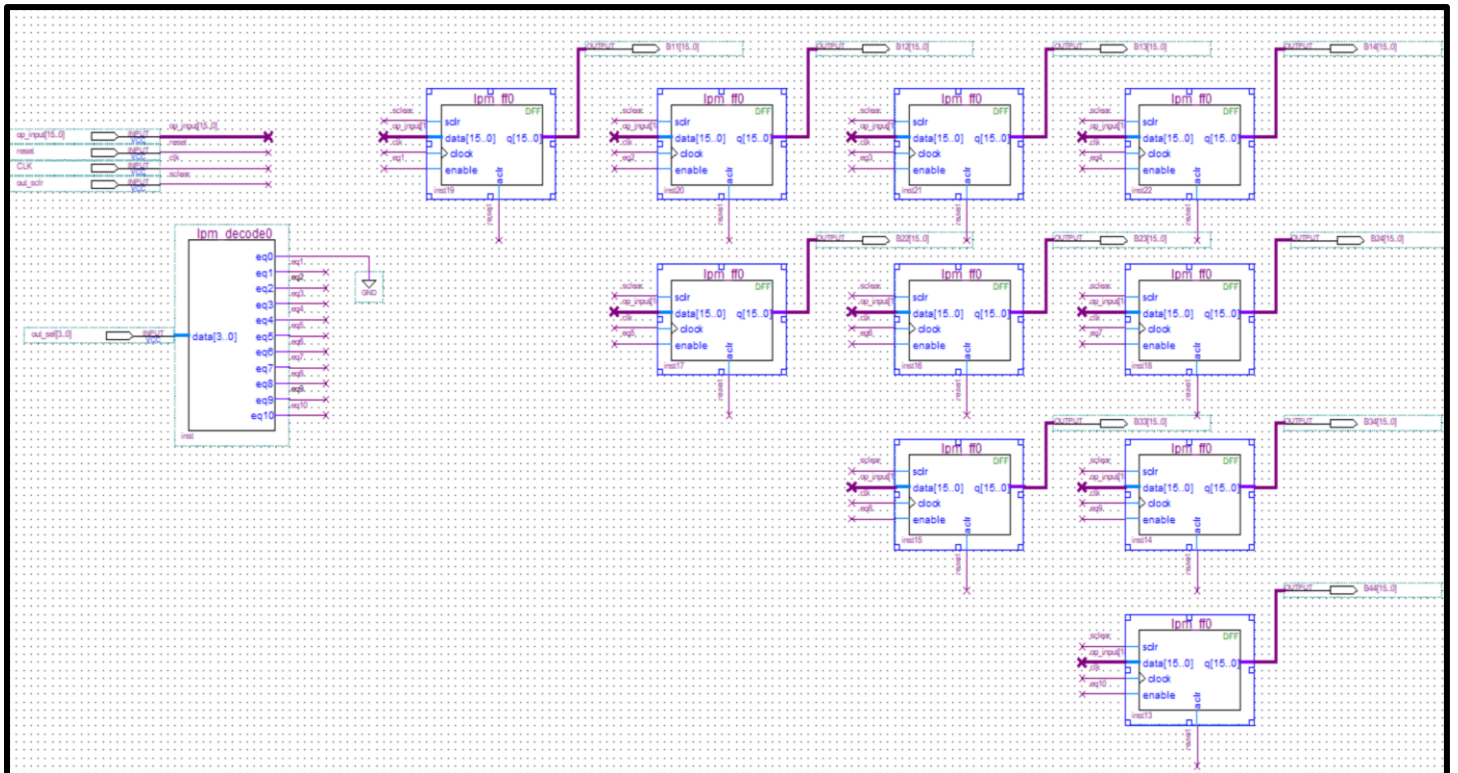


FIG. 6 : OUTPUT REGISTER SCHEMATIC

All the data coming from the MAC goes into goes to the Output Registers which are made up of ten 16-bit D-FF. The decoder is used to select the D-FF in which we store coefficient of the Output matrix.

OUTPUT CONTROLLER VERILOG

```

1 module OUTPUT_CONTROLLER(reset, CLK, cf_load, output_sel, output_rdy);
2
3   input  cf_load, reset, CLK;
4
5   /*control output*/
6   output reg [3:0] output_sel;      //output_sel
7   output reg output_rdy;
8
9   reg [4:0] pstate;                 //current state
10  reg [4:0] nstate;                 //next state
11
12  parameter s0 = 5'b00000, s1 = 5'b00001, s2 = 5'b00010, s3 = 5'b00011,
13            s4 = 5'b00100, s5 = 5'b00101, s6 = 5'b00110, s7 = 5'b00111,
14            s8 = 5'b01000, s9 = 5'b01001, s10 = 5'b01010, s11 = 5'b01011,
15            s12 = 5'b01100, s13 = 5'b01101, s14 = 5'b01110, s15 = 5'b01111,
16            s16 = 5'b10000, s17 = 5'b10001, s18 = 5'b10010, s19 = 5'b10011,
17            s20 = 5'b10100, s21 = 5'b10101, s22 = 5'b10110, s23 = 5'b10111,
18            s24 = 5'b11000, s25 = 5'b11001, s26 = 5'b11010, s27 = 5'b11011,
19            s28 = 5'b11100, s29 = 5'b11101;
20
21  always@(negedge CLK or posedge reset )
22  if (reset == 1'b1)
23    pstate <= s0;
24  else
25    pstate <= nstate;
26
27  always@(pstate or cf_load)
28  begin
29    output_sel [3:0] <= 4'b0;
30    output_rdy <= 0;
31

```

FIG. 7 : OUTPUT REGISTER SCHEMATIC

MATRIX MULTIPLIER DESIGN

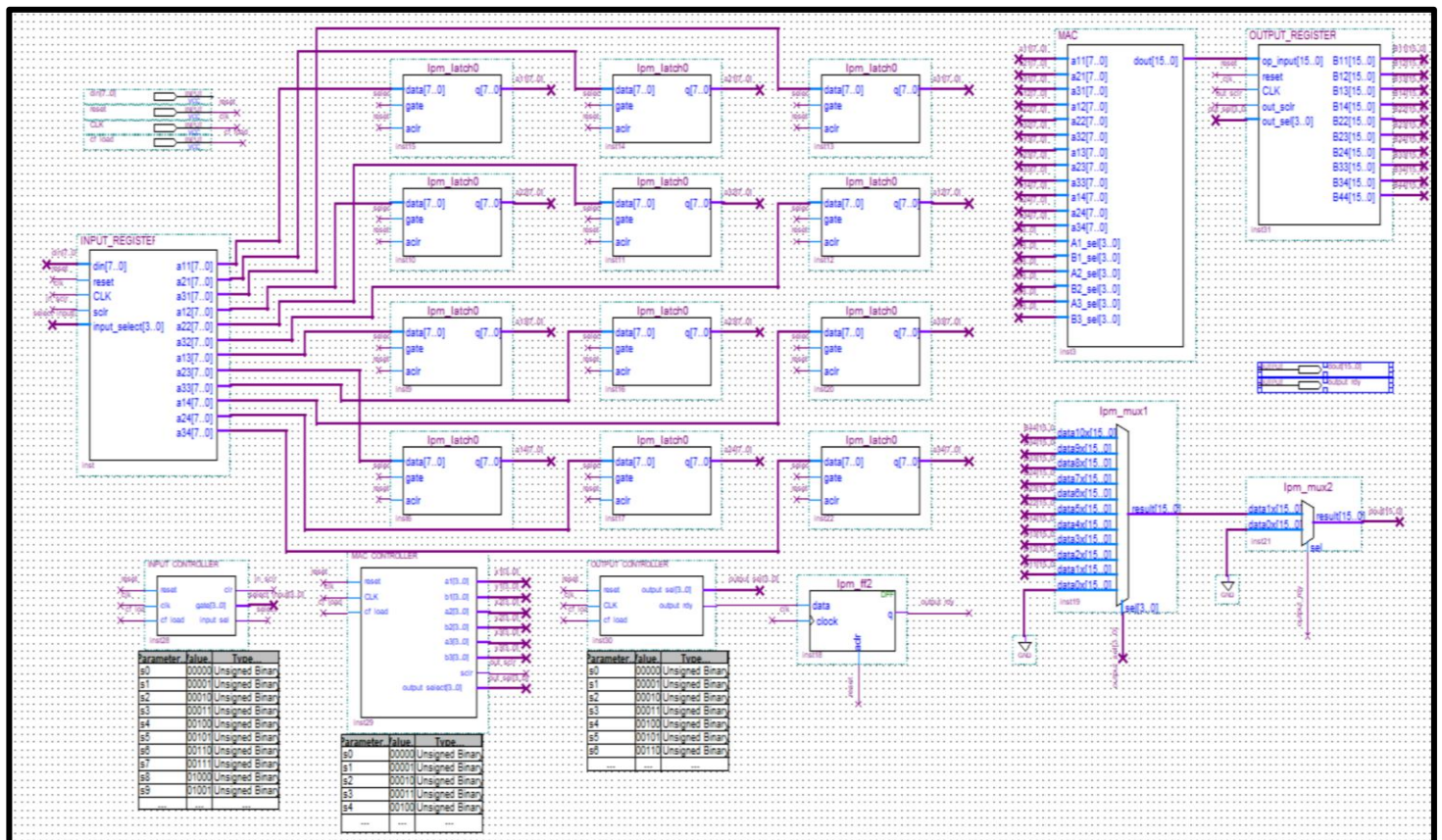


FIG. 8 : MATRIX MULTIPLICATION SCHEMATIC USING CUSTOM DESIGNED SYMBOLS

Functionality Claims

To perform functional test we have to compile and simulate a test bench waveform and match it to the functional requirements and the golden waveform respectively.

Functional requirements for the project are

1. Design must fit within the Altera Cyclone EP1C3T100A8 and the timing analyzer must report at least 45 MHz for the register-to-register delay.
2. Design must fit within the Altera MAXII EPM1270F256A5 and the timing analyzer must report at least 25 MHz for the register-to-register delay.

For Altera Cyclone EP1C3T100A8

SIMULATION REPORT

 


FIG. 9 : SIMULATION REPORT

REGISTER TO REGISTER DELAY REPORT

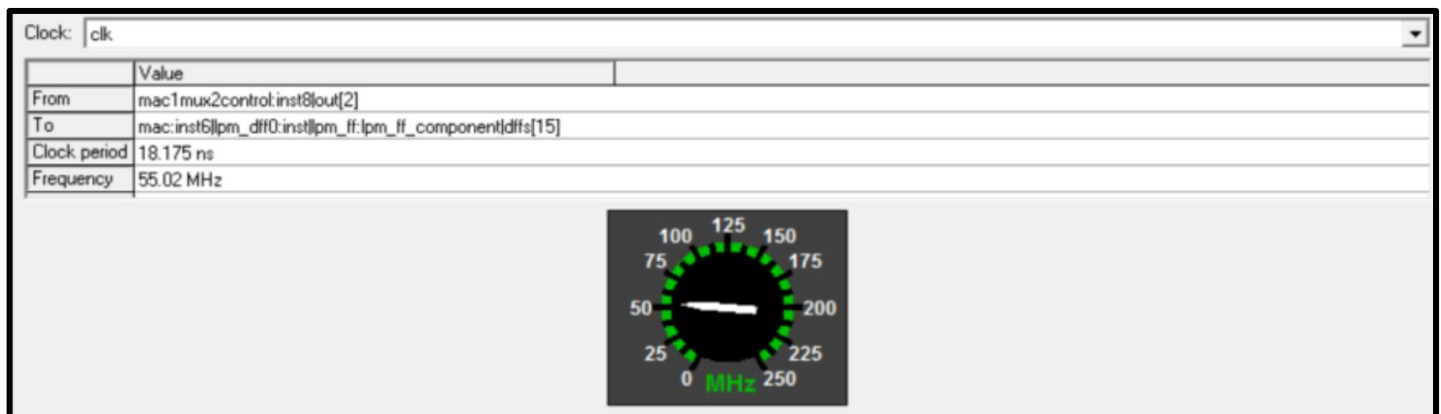


FIG. 10 : REGISTER TO REGISTER DELAY REPORT

For Altera MAXII EPM1270F256A5 SIMULATION REPORT

 


FIG. 11 : SIMULATION REPORT

REGISTER TO REGISTER DELAY REPORT

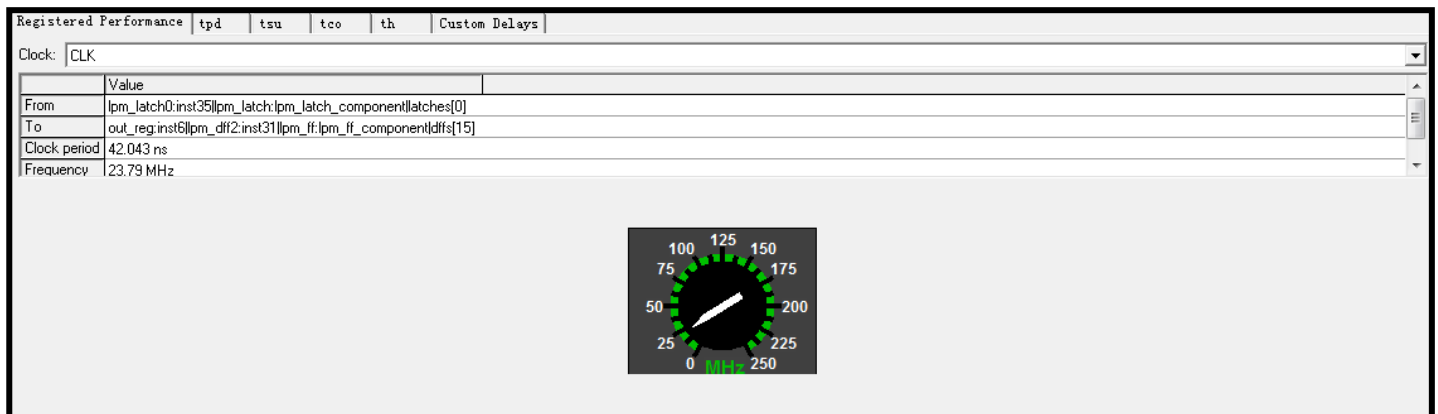


FIG. 12 : REGISTER TO REGISTER DELAY REPORT

ASM CHART INPUT CONTROLLER

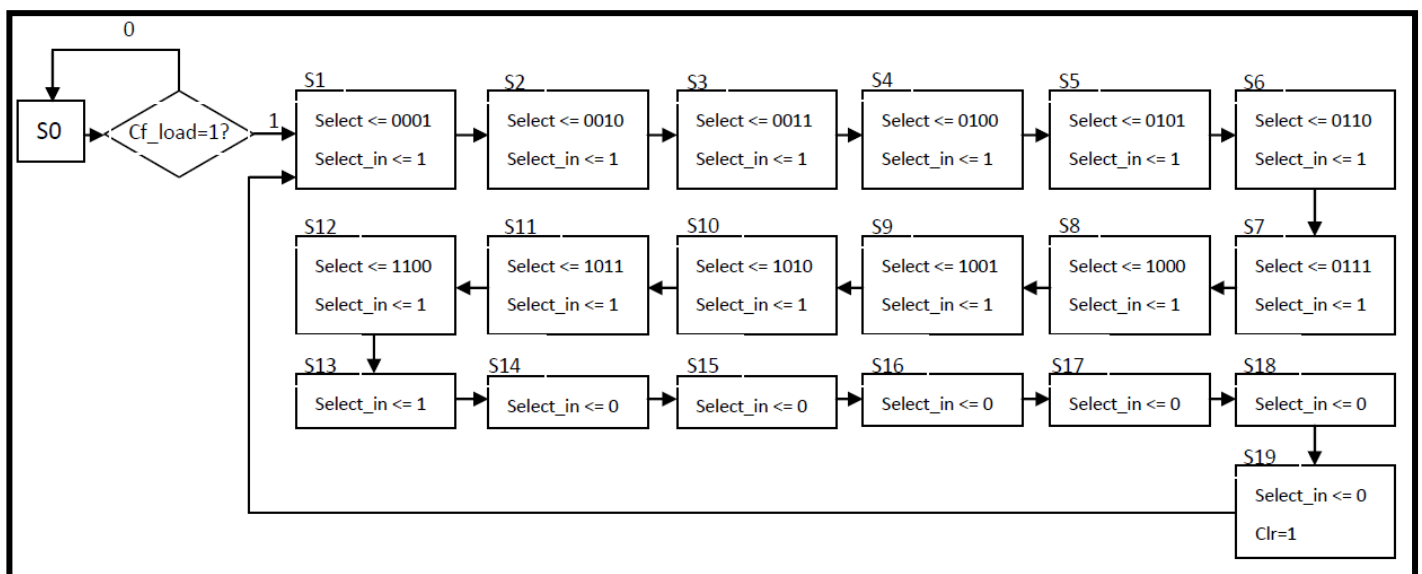


FIG. 13 : ASM CHART FOR INPUT CONTROLLER

MAC CONTROLLER

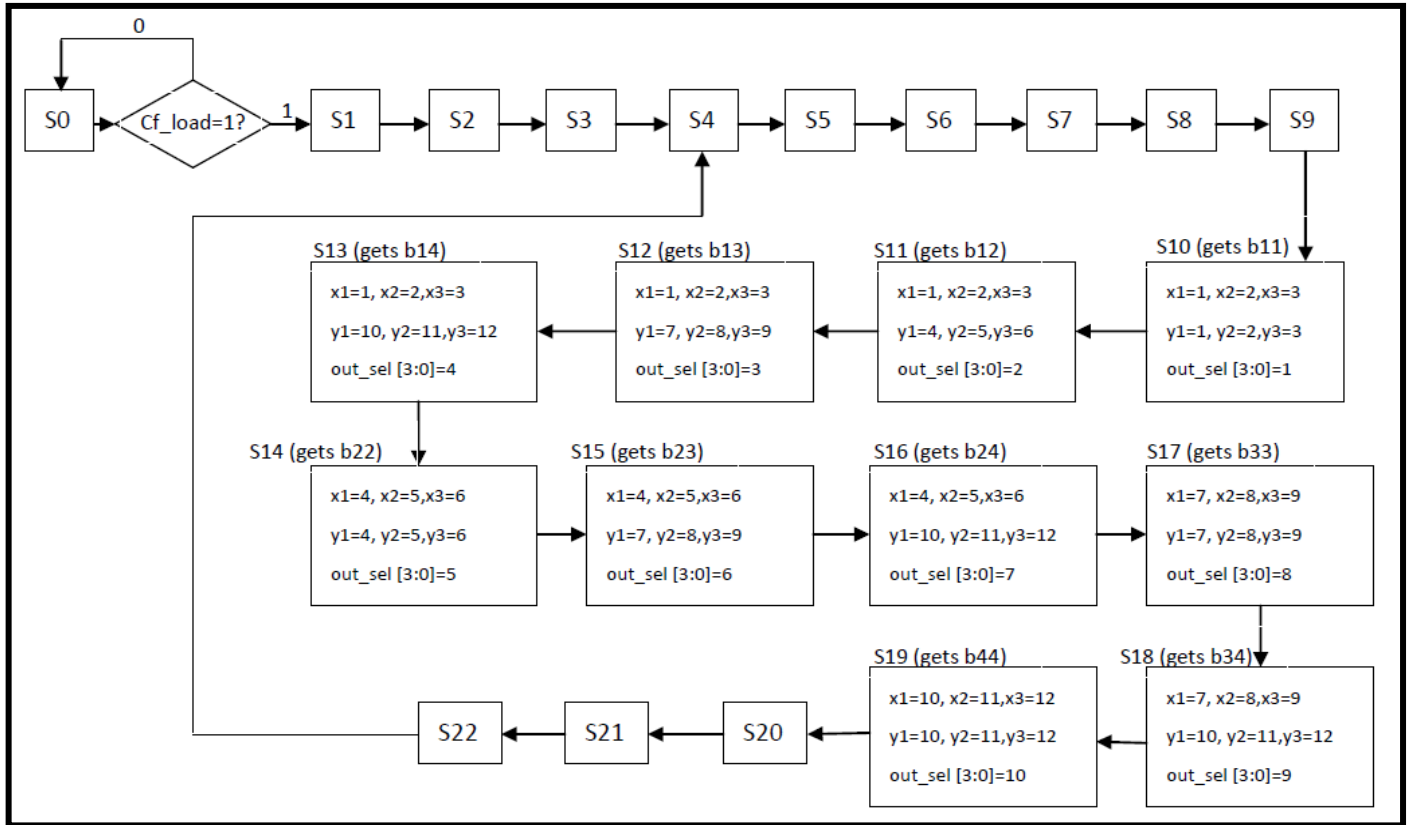


FIG. 13 : ASM CHART FOR MAC CONTROLLER

OUTPUT CONTROLLER

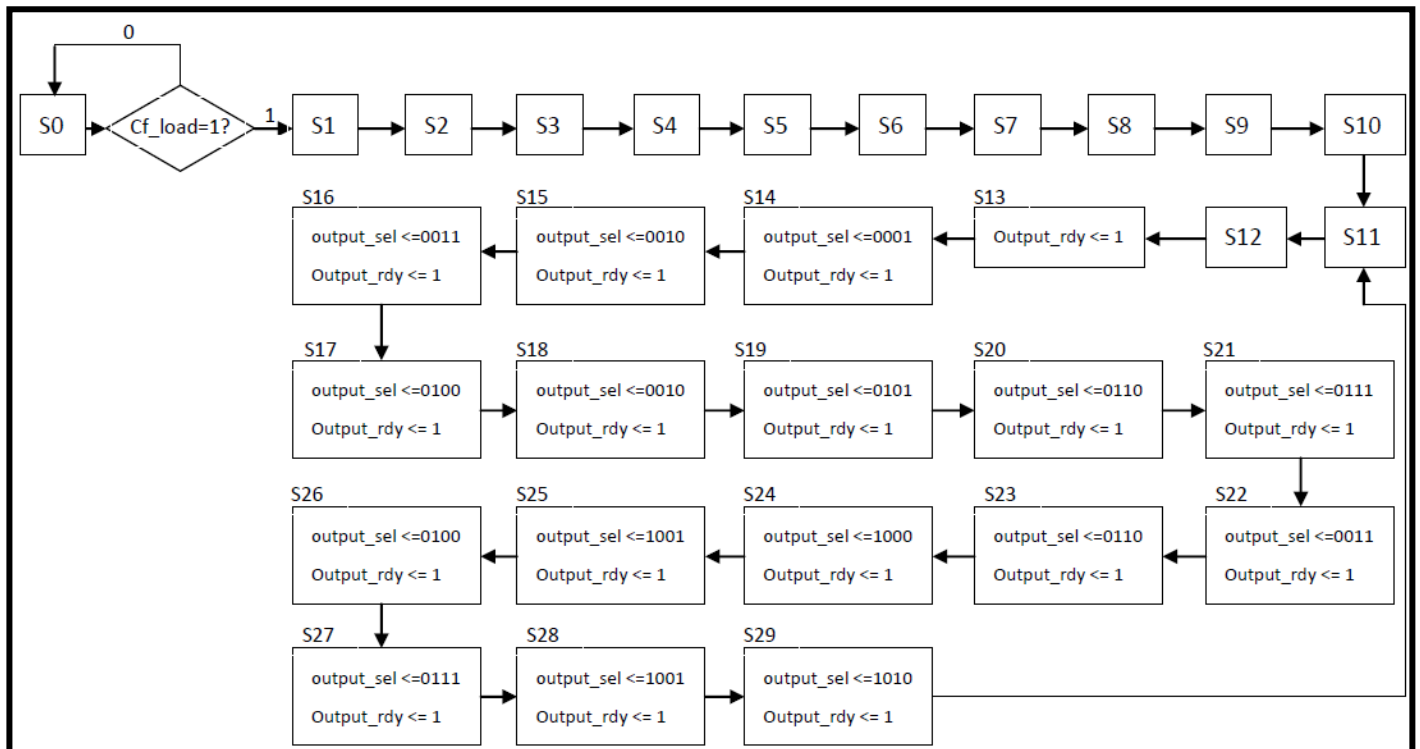


FIG. 13 : ASM CHART FOR OUTPUT CONTROLLER

PROBLEMS FACED

I have tried to solve this project through various ways and have been unsuccessful to get the project match the timing analysis provided in the questionnaire. I found this method of implementation of MAC much easier since it would be loading all data for a single output coefficient at the same time making it easier to make a state machine and clear the flipflops for the new set of inputs at the same time.

CONCLUSION

After detailed analysis and implementation of the project. I am successfully completed the project of performing Matrix Multiplication for a given set of test bench and met the functional requirements provided in the questionnaire.